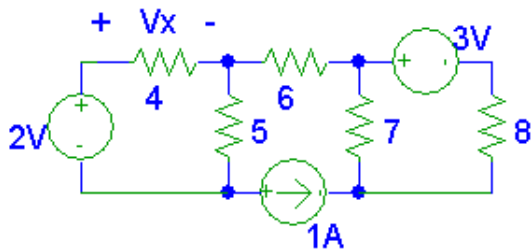


Superposition

[Quick Review of Theory](#)

Example 1




Find the voltage V_x using superposition.

- [Hint](#)
- [Solution](#)



Example 2

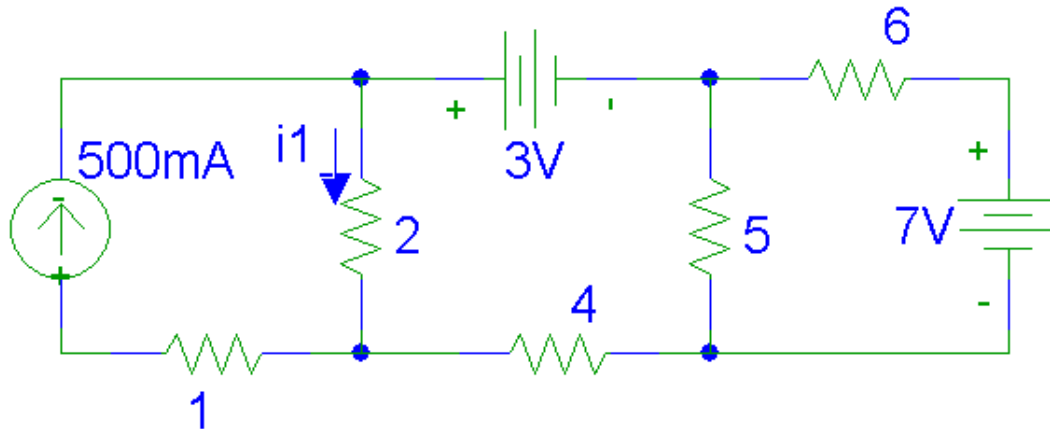


Solve for the current i_1 (through the 2 ohm resistor) in the circuit shown above using superposition

- [Hint](#)
- [Solution](#)




Example 3

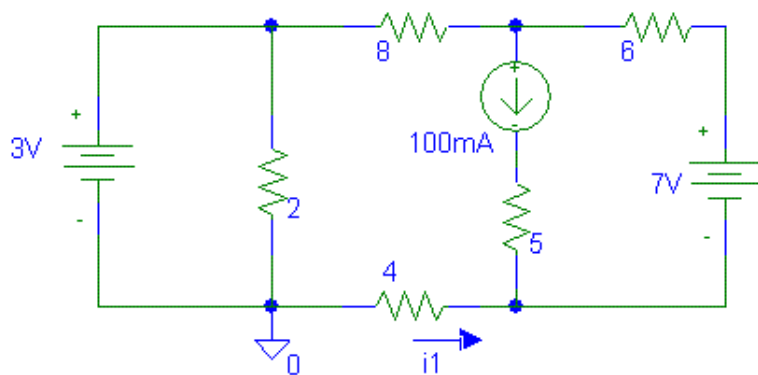

Solve for the current I_1 (through the 4 ohm resistor) in the circuit shown above using superposition.

- [Solution](#) 


Example 4

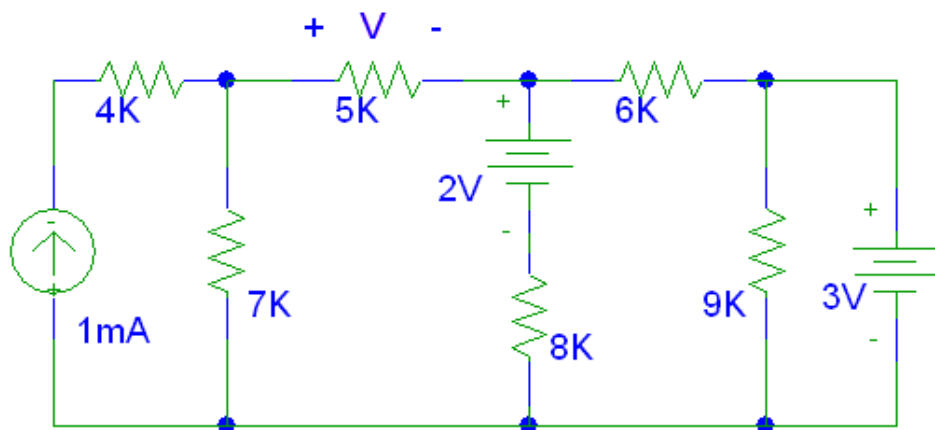

Solve for the voltage V (across the 5 Kohm resistor) in the circuit shown above using superposition .

- [Solution](#) 


Example 5

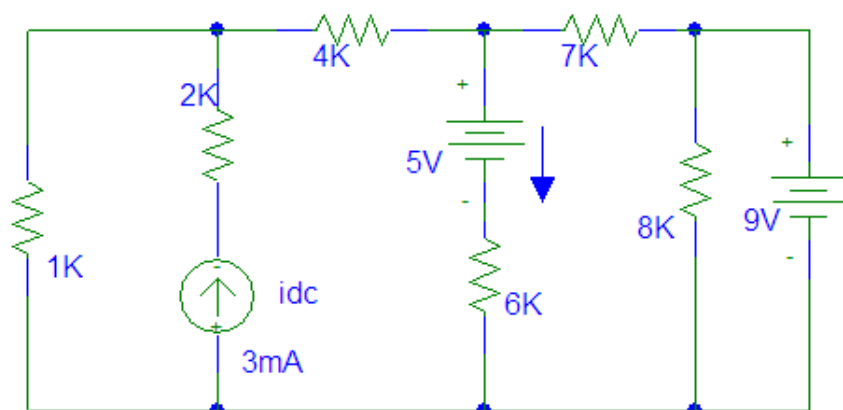

Find the current flowing down through the 5V source in the circuit shown to the left using superposition.

- [Solution](#) 

Example 6

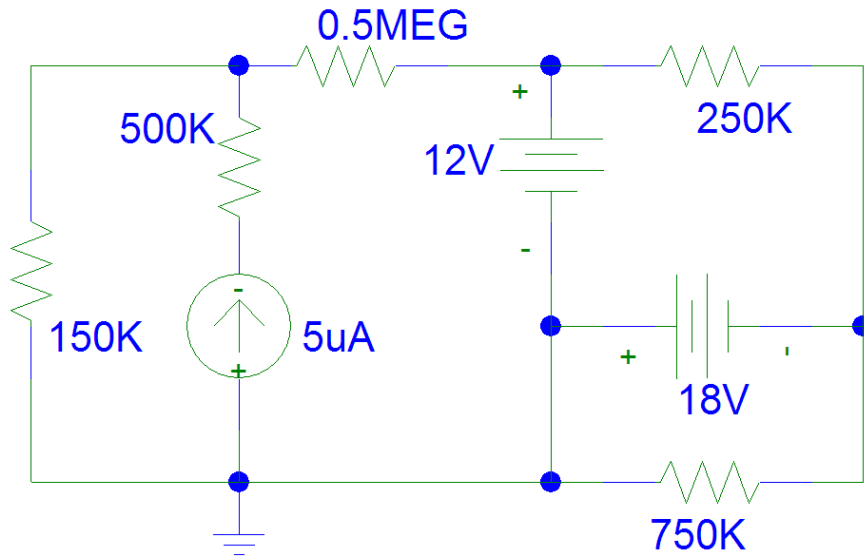


Solve for the voltage over the 150 Kohm resistor (+ on the top, - on the bottom) using superposition.

[Solution](#)



Example 7

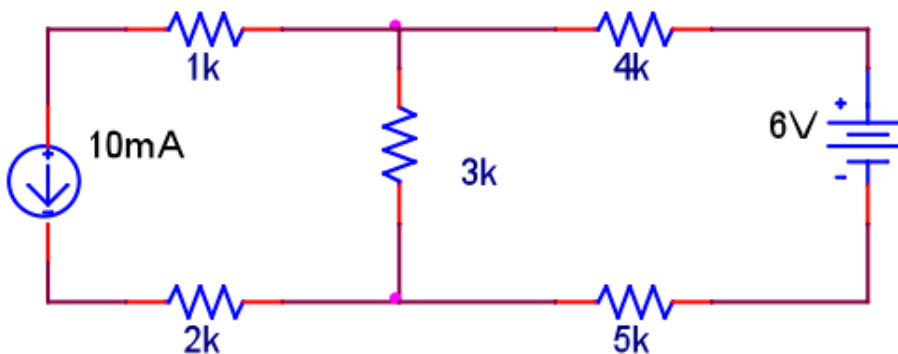


Use superposition to find the current flowing downward through the 3Kohm resistor.

[Solution](#)



Example 8

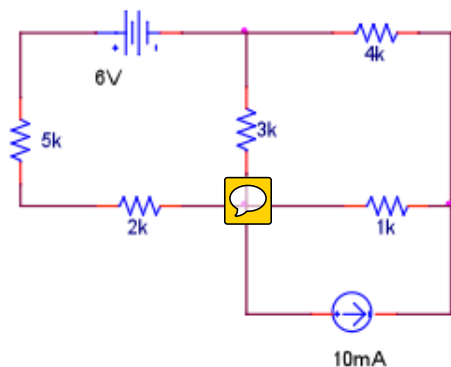


Use superposition to find the power absorbed by the 2K resistor and the 10mA source in the circuit shown above.

[Solution](#)



Example 9

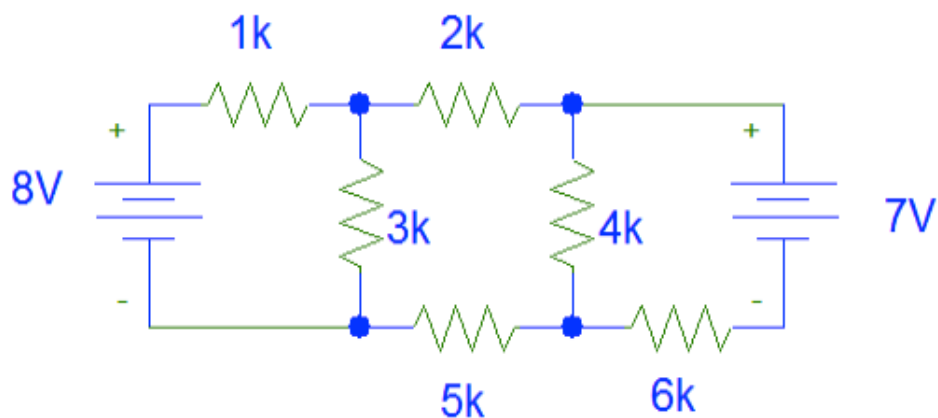


Solve for the current flowing right through the 2 K resistor in the circuit shown below, using superposition.

[Solution](#)



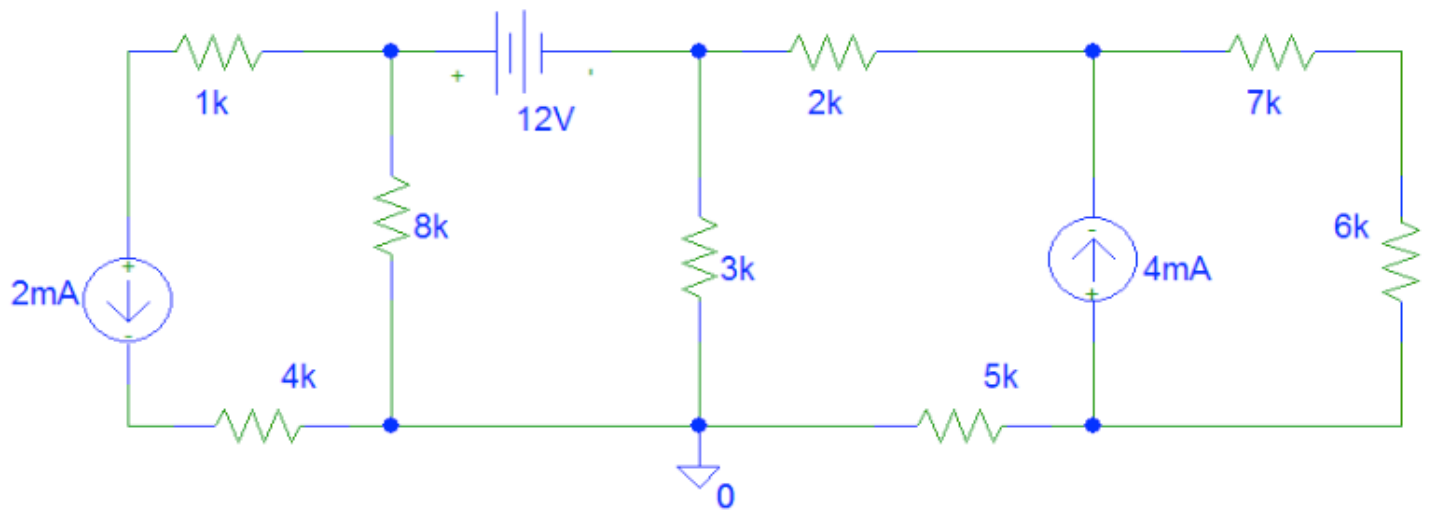Example 10

Solve for the current flowing down through the 3K ohm resistor in the middle of the circuit using superposition.



Solution

(c) 2014, Steven H. VanderLeest